

# Project Overview: Digital Clock

---

## • What It Is:

A **digital clock** built using **basic digital electronics components**—specifically **logic gates** (AND, NOT, etc.) and **J-K flip-flops**—which counts and displays time in hours, minutes, and seconds.

This type of clock **does not use a microcontroller** or advanced processors. Instead, it relies on **discrete logic** to perform counting and display operations.

---

## • How It Works:

### ○ Counting Time with J-K Flip-Flops

The time is divided into three main counting sections:

#### 1. Seconds Counter (00–59)

A series of J-K flip-flops is configured to count from 0 to 59. Once the count reaches 60, the circuit resets the seconds counter to 00 and sends a pulse to the next counter.

#### 2. Minutes Counter (00–59)

Another chain of J-K flip-flops counts minutes, incrementing by one each time the seconds counter resets. This counter also resets at 60 and triggers the hours counter.

#### 3. Hours Counter (00–12)

The final stage counts the hours in a 12-hour format. Once it reaches 12, it resets back to 00.

### ○ Control with Logic Gates

Logic gates (AND, NOT, etc.) are used to:


- Detect when a counter reaches its maximum value (like 59 or 12).
- Reset counters to zero at the correct time.
- Generate carry-out signals to trigger the next stage in the chain.

### ○ Displaying the Time


The binary output from each counter is connected to a 7-segment decoder, which converts the binary values into signals for a 7-segment display. This allows the current time to be shown in the format HH:MM:SS using 7 segment displays.

---


## • Simulation

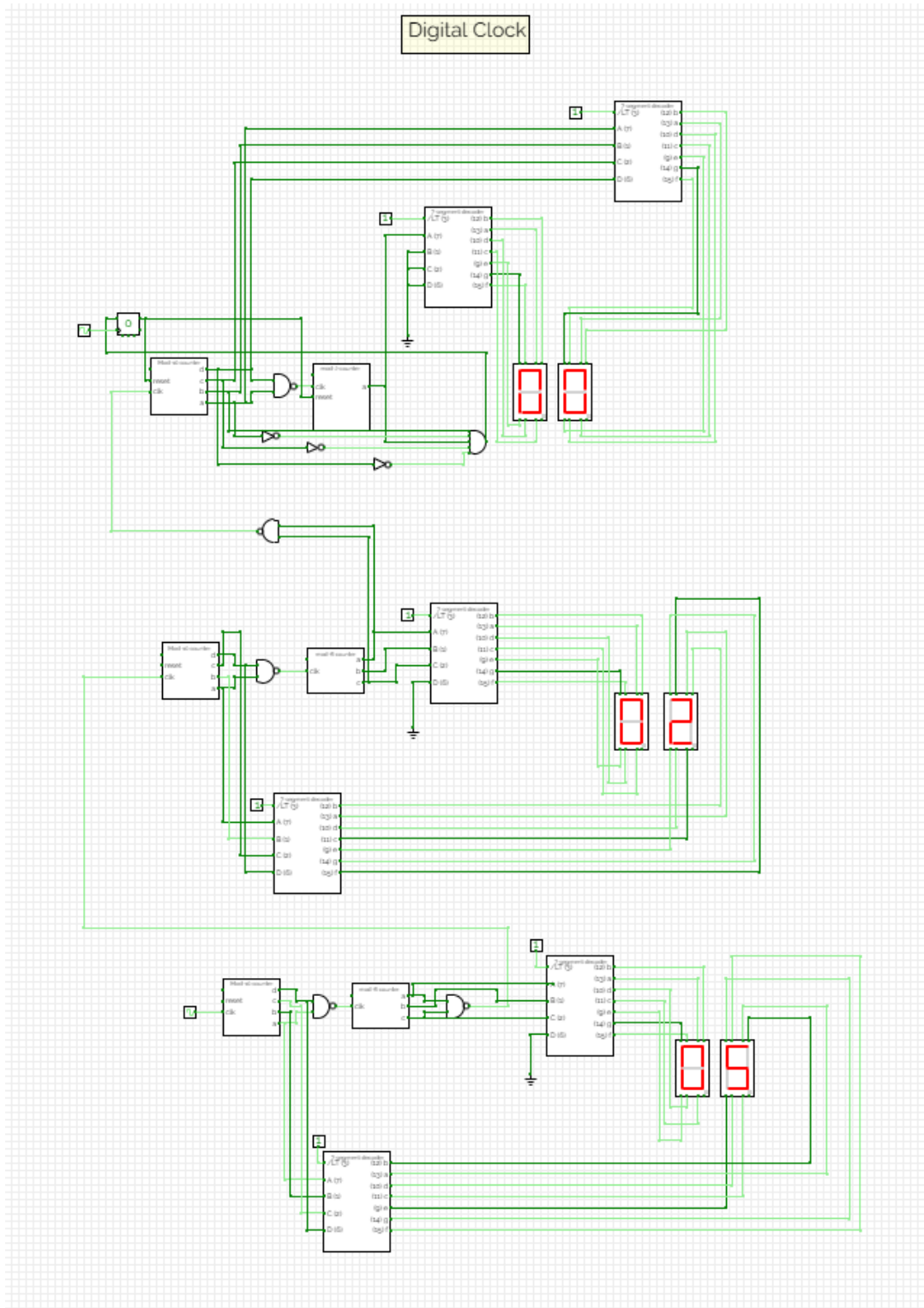


Mod-10 counter

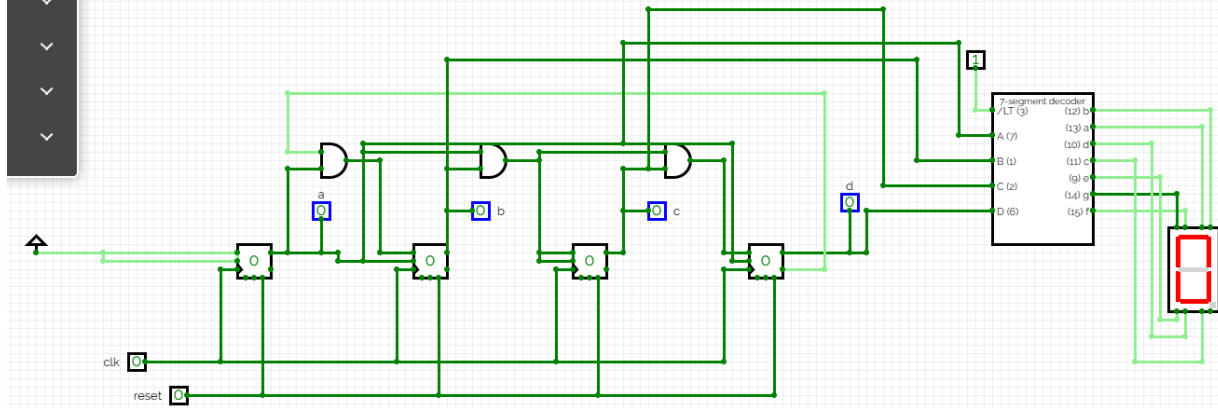

Mod-6 counter

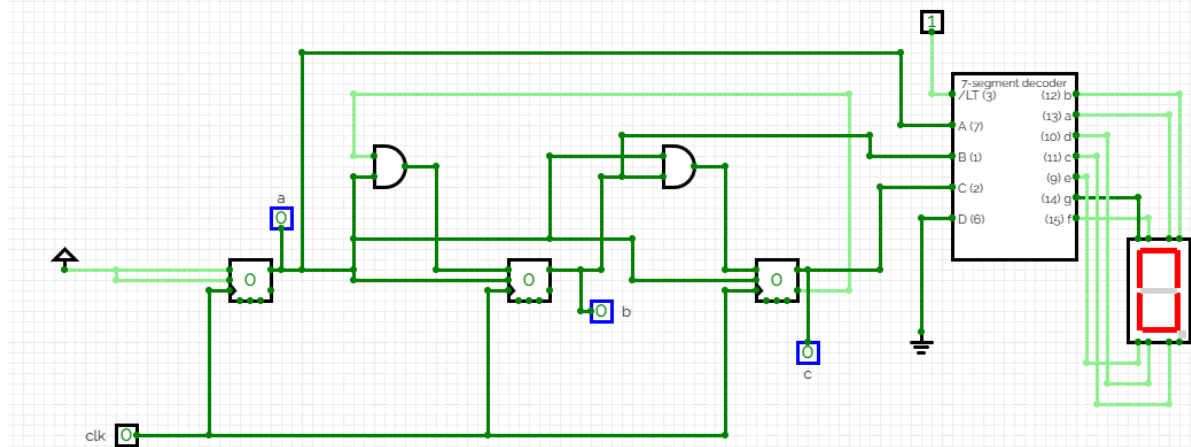

# Mod-2 counter

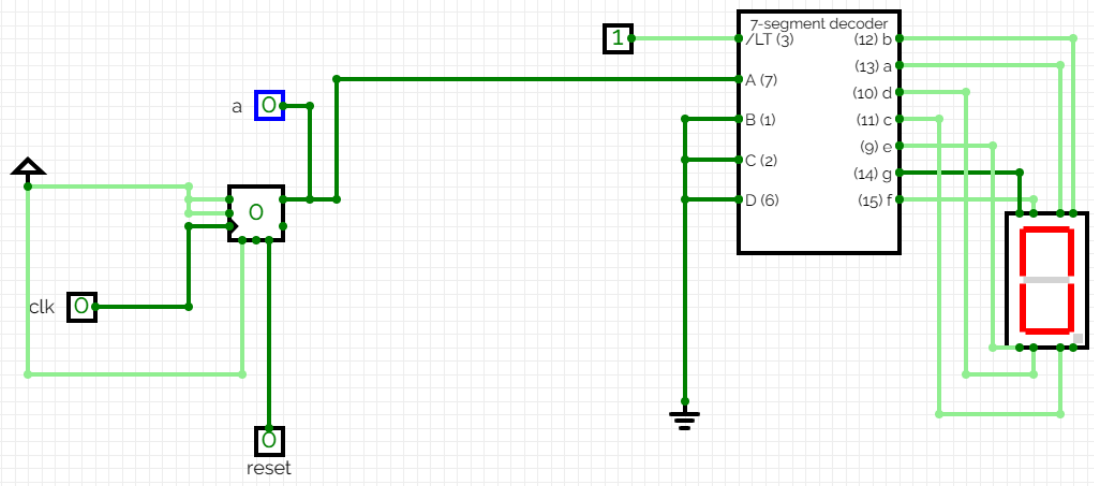

# • State Table and logical function

GHARIB Mod-6 counter

Present state			Next state								
$^a C$	$^a B$	$^a A$	$^a C$	$^a B$	$^a A$	$J_C$	$K_C$	$J_B$	$K_B$	$J_A$	$K_A$
0	0	0	0	0	1	0	X	0	X	1	X
1	0	1	0	1	0	0	X	1	X	X	1
2	0	1	0	1	1	0	X	X	0	1	X
3	0	1	1	1	0	0	1	X	1	X	1
4	1	0	0	1	0	1	X	0	X	1	X
5	1	0	1	0	0	X	1	0	X	X	1
6	1	1	0	X	X	X	X	X	X	X	X
7	1	1	1	X	X	X	X	X	X	X	X
8	X	X	X	X	X	X	X	X	X	X	X
9	X	X	X	X	X	X	X	X	X	X	X

$A$

0	1	1	1	0
1	0	1	0	1

$B$

$K_A = 1$

$A$

1	X	X	1
1	X	X	X

$J_A = 1$

$A$

X	X	1	0
X	X	X	X

$B$

$K_B = A$

$A$

X	X	X	X
0	1	X	X

$B$

$K_C = A$

$A$

0	0	1	0
X	X	X	X

$B$

$J_C = AB$

$A$


0	1	X	X
0	0	X	X

$B$

$J_B = AC$



Present state				Next state				Mod-10 Counter							
D	C	B	A	D <sub>n+1</sub>	C <sub>n+1</sub>	B <sub>n+1</sub>	A <sub>n+1</sub>	J <sub>D</sub>	K <sub>D</sub>	J <sub>C</sub>	K <sub>C</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>A</sub>	K <sub>A</sub>
0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
1	0	0	1	1	0	0	0	X	1	0	X	0	X	X	1
1	0	1	0	X	X	X	X	X	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X	X	X	X	X

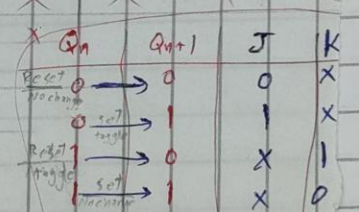

x	1	1	x
x	1	1	x
x	x	x	x
x	1	x	x

$K_A = 1$

1	x	x	1
1	x	x	1
x	x	x	x
1	x	x	x

$J_A = 1$

x	x	1	0
x	x	1	0
x	x	x	x
x	x	x	x

$K_B = A$

0	1	x	x
0	1	x	x
x	x	x	x
0	0	x	x

$J_B = A\bar{D}$

x	x	x	x
0	0	1	0
x	x	x	x
x	x	x	x

$K_C = AB$

0	0	1	0
x	x	x	x
x	x	x	x
0	0	x	x

$J_C = AB$

x	x	x	x
x	x	x	x
x	x	x	x
0	1	x	x

$K_D = A$

0	0	0	0
0	0	1	0
x	x	x	x
x	x	x	x

$J_D = ABC$

